

Homework 3

Problem 3.1

Solution:

A) Distributive rule: $(M + N)(!M + P)(!N + !P) = (M * !M + P * M + N * !M + NP)(!N + !P)$

Complement:

$$(M * !M + P * M + N * !M + NP)(!N + !P) = (P * M + N * !M + NP)(!N + !P)$$

Distributive rule:

$$(P * M + N * !M + NP)(!N + !P) = (!N * P * M + !N * N * !M + !N * N * P + !P * P * M + !P * N * !M + !P * N * P)$$

Complement:

$$(!N * P * M + !N * N * !M + !N * N * P + !P * P * M + !P * N * !M + !P * N * P) = (!N * P * M + !P * N * !M)$$

B) Distributive rule:

$$!A * B * !C + A * B * !C + B * !C * D = B * !C * (!A + A + D)$$

Complement:

$$B * !C * (!A + A + D) = B * !C * (1 + D)$$

De morgan:

$$B * !C * (1 + D) = B * !C$$

C) De morgan:

$$!((M + N + P) * Q) = !(M + N + P) + !Q$$

DE morgan and associative:

$$!(M + N + P) + !Q = !M * !N * !P + !Q$$

d) De morgan and associative:

$$!((A * B * C) + (D * E * F)) = !(A * B * C) * !(D * E * F)$$

De morgan and associative:

$$(!A + !B + !C) * (!D + !E + !F)$$

e) De morgan and associative:

$$!((A * !B) + (C * !D) + (E * F)) = !(A * B) * !(C * !D) * !(E * F) =$$

De morgan and associative:

$$(!A + !B) * (!C + D) * (!E + !F)$$

f) De morgan and associative:

$$!(A + B * !C) + D * !(E + !F) = (A + B * !C) * !(D * !(E + !F)) =$$

De morgan and associative:

$$(A + B * !C) * (!D + (E + F))$$

Problem 3.2

Solution:

By observing the given circuit we can conclude that it corresponds to the following expression:

$$(\overline{A} * \overline{B} * \overline{C}) + (A * \overline{B} * \overline{C}) + (\overline{A} * \overline{B} * D)$$

Constructing the table:

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	1	1	1	0
$\overline{A}B$	0	0	0	0
AB	0	0	0	0
$A\overline{B}$	1	1	0	0


From this we can conclude we have 2 unique loops:

(0,0),(0,1),(3,0),(3,1)

(0,1), (0,2)


Therefore the equation is $\overline{B} * \overline{C} + \overline{A} * \overline{B} * D$

Solution:

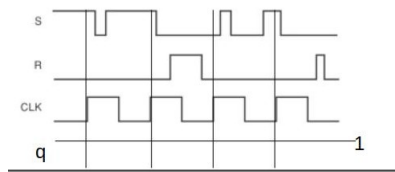


S	R	CLK	Q
0	0	UP	Q_0
1	0	UP	1
0	1	UP	0
1	1	UP	Ambiguous

Solution:

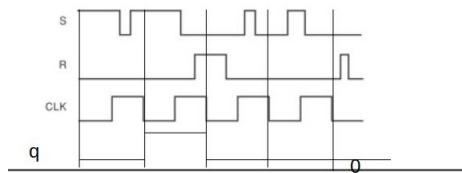


S	R	CLK	Q
0	0	DOWN	Q_0
1	0	DOWN	1
0	1	DOWN	0
1	1	DOWN	Ambiguous

Solution:

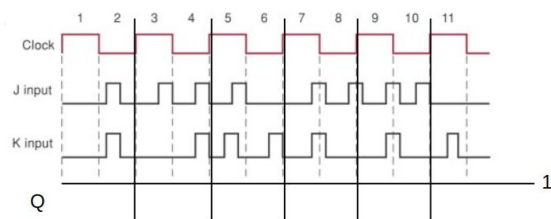

S	R	CLK	Q
0	0	UP	Q_0 (No change)
1	0	UP	1
0	1	UP	0
1	1	UP	$\overline{Q_0}$ (toggles)

Solution:

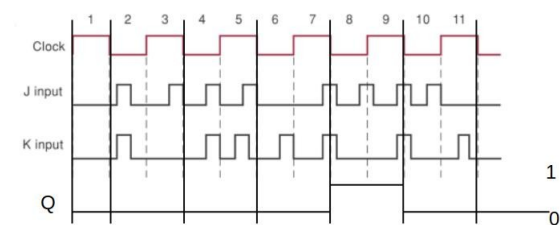


J	K	CLK	Q
0	0	DOWN	Q_0 (No change)
1	0	DOWN	1
0	1	DOWN	0
1	1	DOWN	$\overline{Q_0}$ (toggles)

Problem 3.7

Solution:

A) Let's start analyzing from the back. We want Y to get HIGH. We observe that it is a J-K flip flop, with grounded K. That means $K = 0$ for ever. Assuming the flip flop react on the positive going transitions, we want scenario where input J is HIGH, and timer to react after it, noticing the change. So what we want is J,C going high in this order. (According to state table from previous exercises). IN order J to get HIGH, we want X to get high. For that the situation is indentical, so we want to get A, then B HIGH, so we can register the change, and output HIGH at X, that will go to another J, and C will get HIGH, and after that Y will end up being high. So the order is A, B, C.

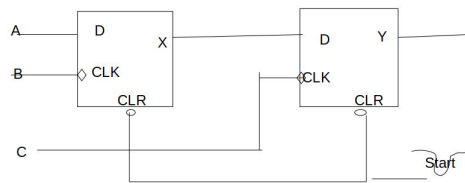B) Since, the signal is connected to the CLR asynchronous input, it makes the X and Y outputs 0, it wipes it immediately. It is low input, so low start will set outputs to 0, "restarting" them.



C)